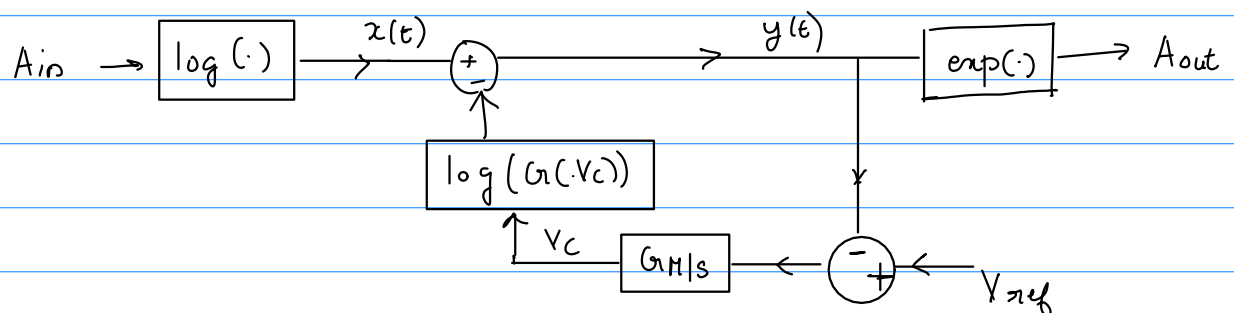



Not required to be submitted.  
Review before final exam.

## AV314 - Assignment 8

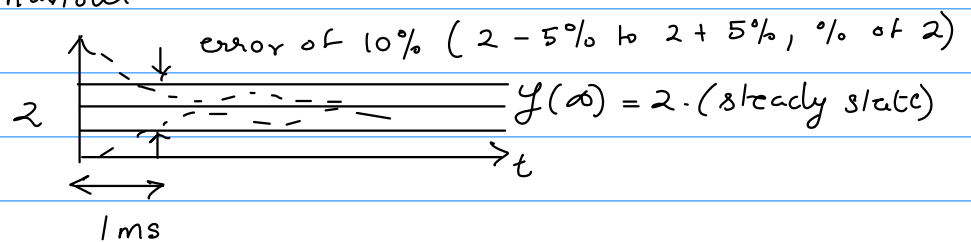- 1) Draw the block diagram of an AGC loop which is used to automatically control the average power of a signal, so that the signal put out from the AGC loop has a constant power.
- 2) The AGC loop that was discussed in class was:



Assuming that  $G(V_c) = e^{aV_c}$ , design  $a$ ,  $G_H$ , and  $V_{ref}$  so that  $y(t)$  has the following behaviour.



The  $y(t)$  response should converge to the interval as shown above in 1 ms.